

Early Output Logic with Anti-Tokens

Charlie Brej, Jim Garside

APT Group

Manchester University



Outline

Asynchronous Logic

- DIMS (Delay Insensitive Minterm Synthesis)

Early Output Logic

- Guarding



Anti-Tokens

- Collisions


Conclusions




Asynchronous Latch

 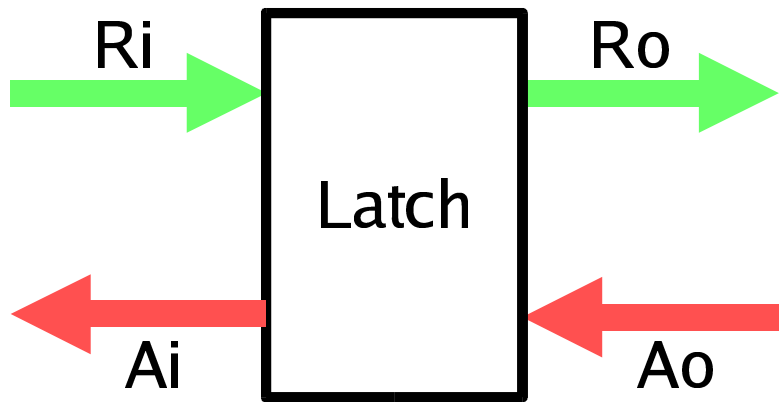

Asynchronous Pipeline

 

Asynchronous Pipeline Stall

 

Dual-Rail Latch

Dual-Rail


00 = 'NULL'

01 = 0


10 = 1

11 = Illegal


Return to 'NULL'

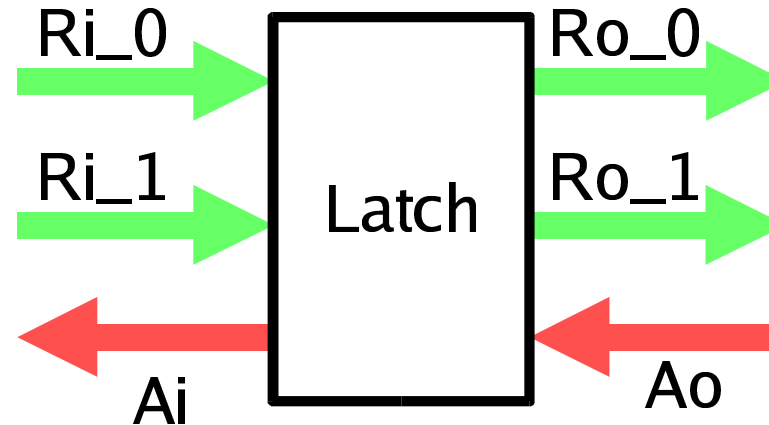

DIMS Logic

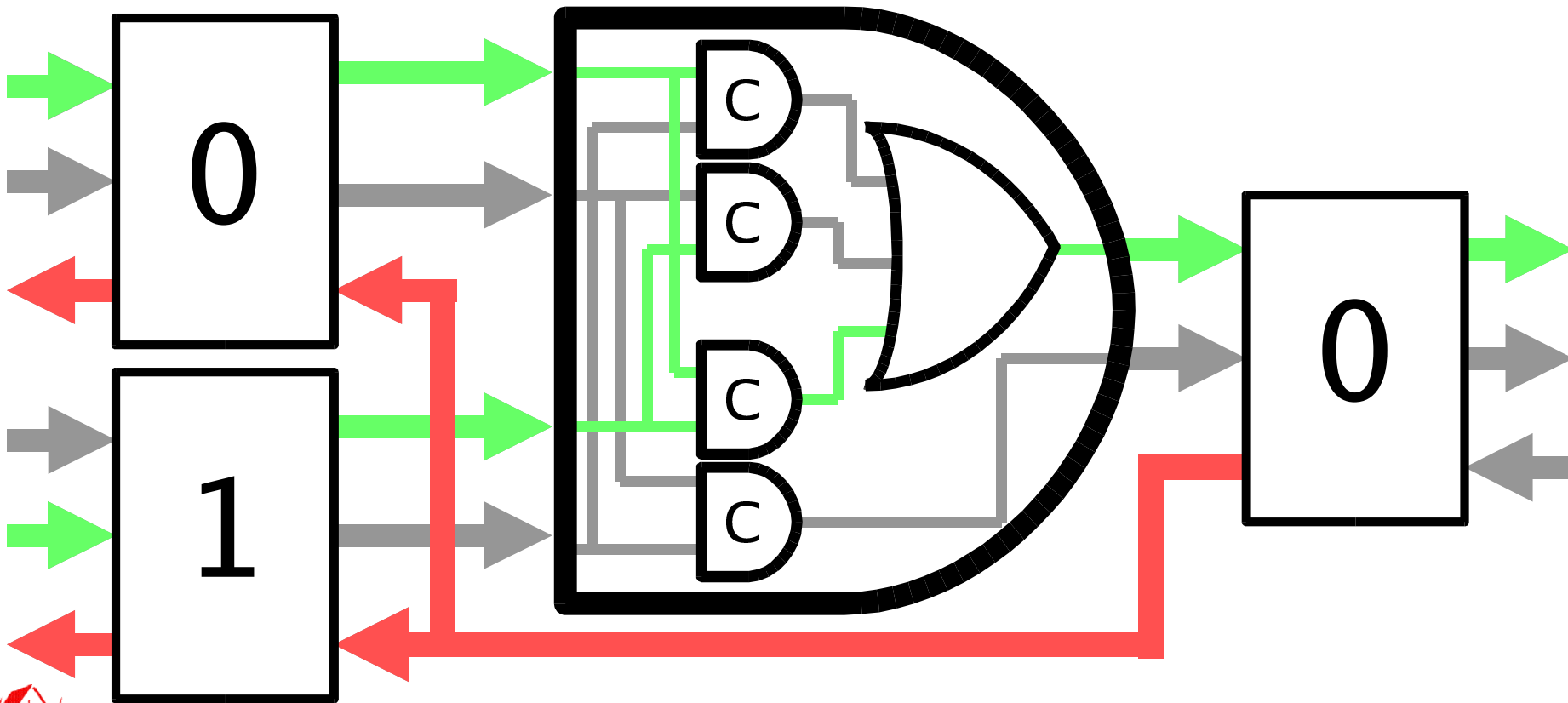


DIMS vs Early Output Logic

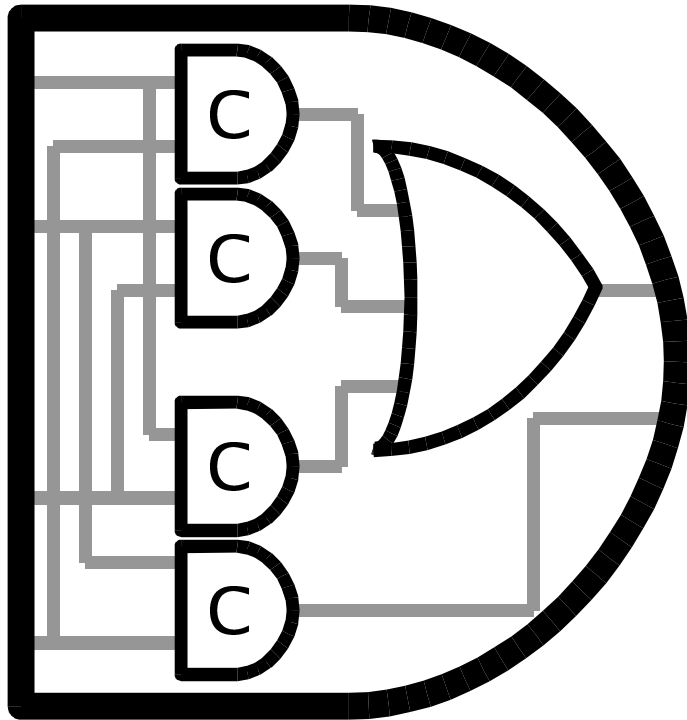

Size:48 transistors

Delay:4 inversions

 


Size:12 transistors

Delay:2 inversions



Early Output Logic

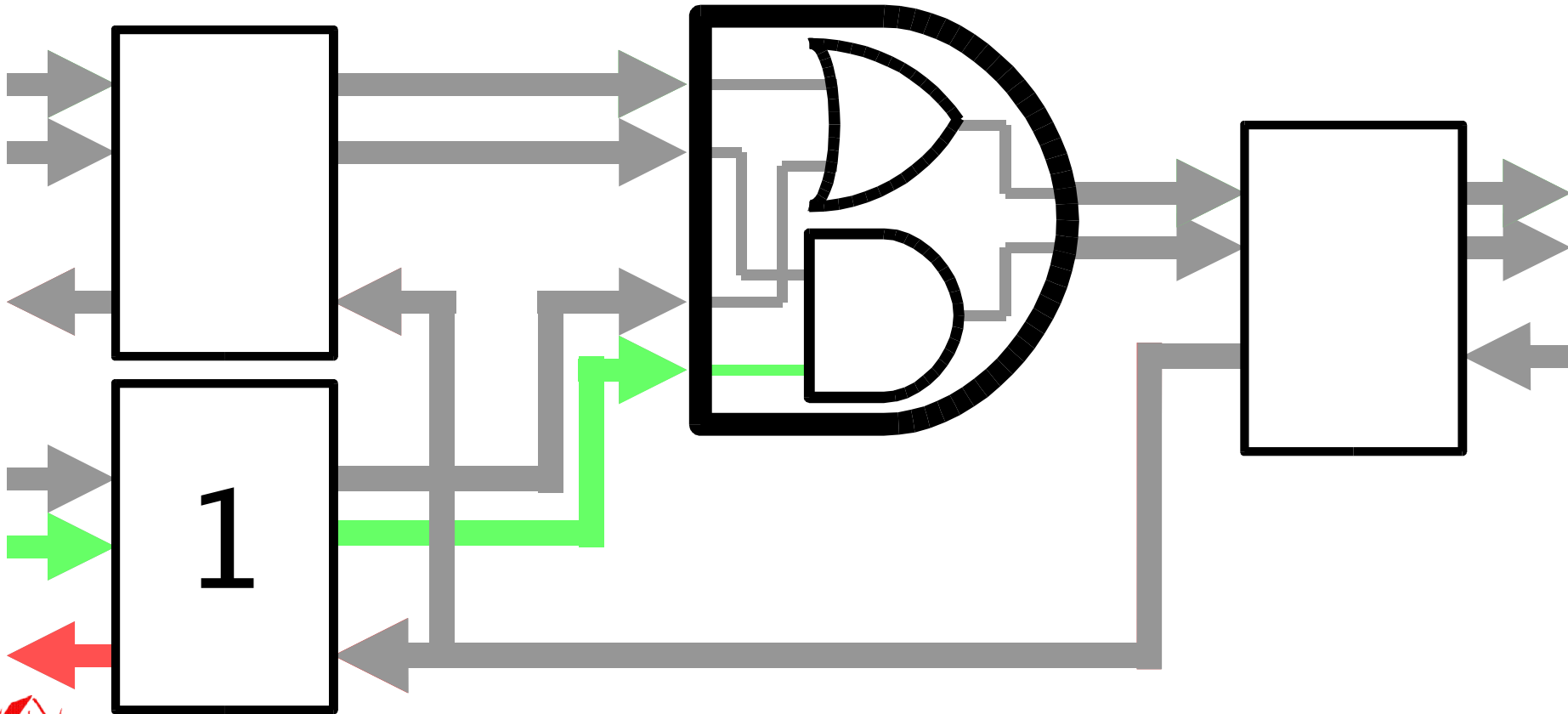

Guarding

Problem:

Inputs


Late

Unnecessary


Acknowledge before ready

Solution:

Validity signal (V_o)

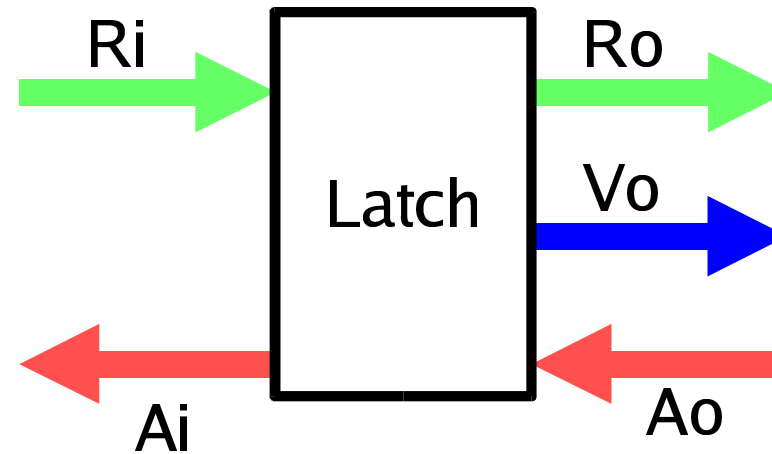

Early Output Guarding

 

Anti-Tokens

Don't:

- Stall entire stage until late input arrives

Do:


- Stall the latch instead

 - Early 'Validity'


 - Acknowledge before Data




Anti-Token Generation

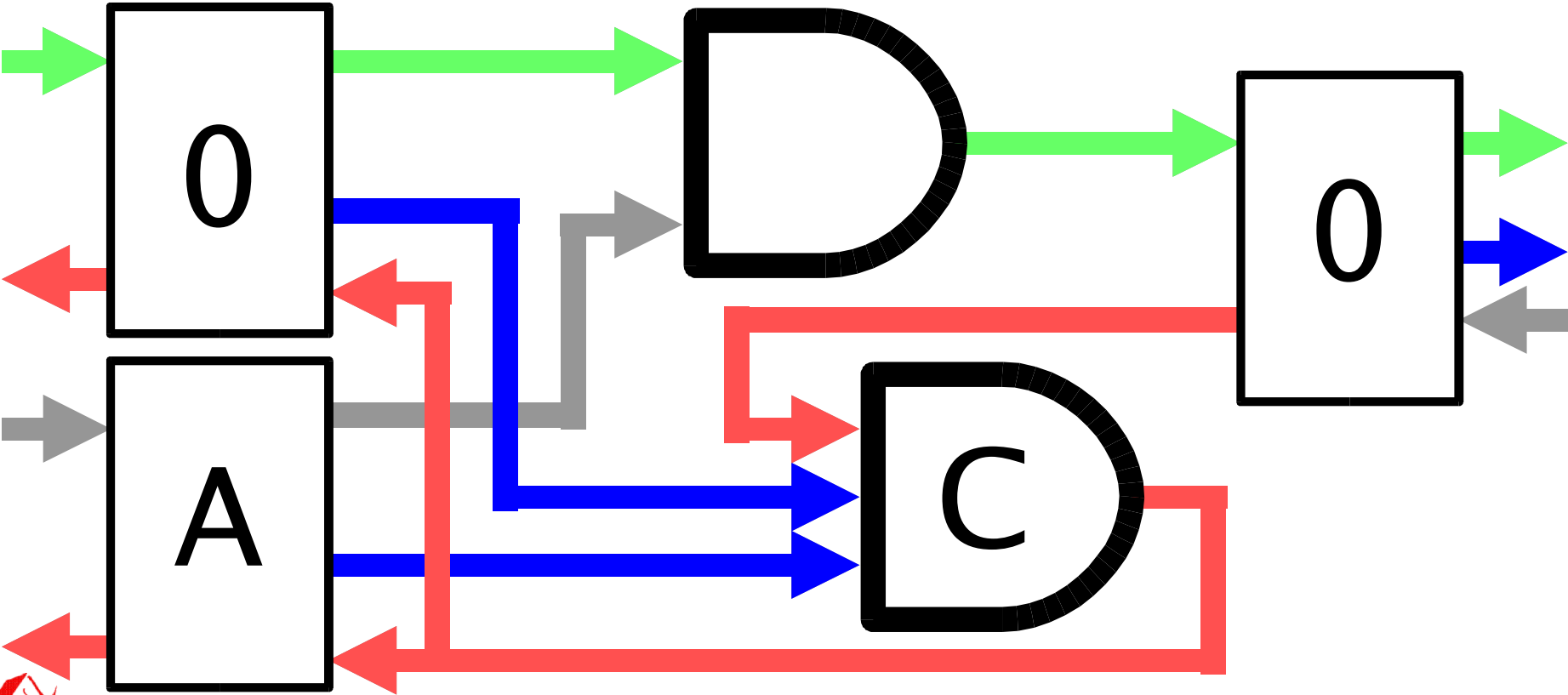


Anti-Token Propagation

 


Token Pass

 


Anti-Token Pass

 

Token Anti-Token collision

 

Token Anti-Token collision 2

 

Dual-Purpose Signals

Arbiter free

Req:


- Token Request

- Anti-Token Acknowledge

Ack:

- Anti-Token Request

- Token Acknowledge

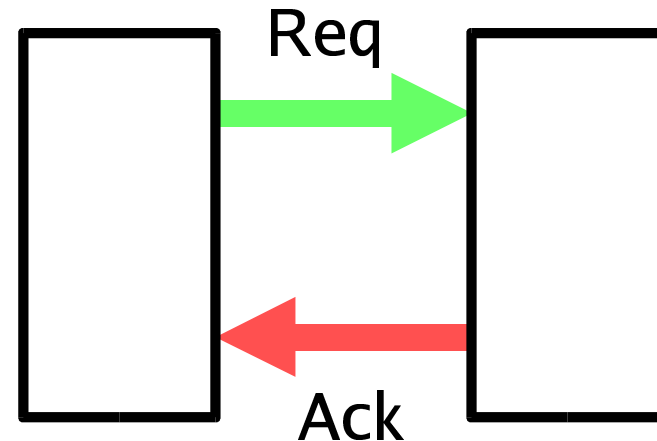

Conclusions

- New, fine-grain, asynchronous pipeline
- Faster than DIMS (2x)
- Smaller than DIMS (4x)
- Lower power than DIMS
- Some speed advantages over synchronous designs
- Counterflow - no arbitration
- Requires some timing assumptions



Timing Hazard example

